

Total No. of printed pages = 4

EI 181303

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

BINA CHOWDHURY CENTRAL LIBRARY

(CSE & IIS)

SVKM's Institute of Technology

Warananasi, Kolkata - 713017

25/12/2021

B.Tech. 3<sup>rd</sup> Semester End-Term Examination

EE, IE

ANALOG ELECTRONICS

(New Regulation & New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Question No. 1 is compulsory. Answer either Part (a) or (b) from the rest.


1. Fill in the blanks : (10 × 1 = 10)
- (a) If the current in an intrinsic conductor for an applied voltage of 5V, is 10  $\mu$ A at 30°C, the current that would flow at 20°C for the same applied voltage will be \_\_\_\_\_.
- (b) The Base Current for a PNP transistor is 40  $\mu$ A, while the Collector Current is 20 mA. The value of  $\beta$  for the transistor is \_\_\_\_\_.
- (c) The r-parameter Model of a BJT is derived from \_\_\_\_\_ model.
- (d) A JFET is operating in \_\_\_\_\_ region when the Drain-Source voltage  $V_{DS} < V_p$ .
- (e) Voltage-Series Negative Feedback applied to an OPAMP results in \_\_\_\_\_ configuration of an OPAMP amplifier.

Answer True or False

- (f) Simple Shunt Capacitor Filter results in the reduction of ripple completely.
- (g) A transistor is always operated in the Active Region for amplifiers.
- (h) VMOS is most suitable for a Power Switch.
- (i) OPAMPs are always operated in the Inverting Mode.
- (j) Active Filters with OPAMP always show the best results.

[Turn over

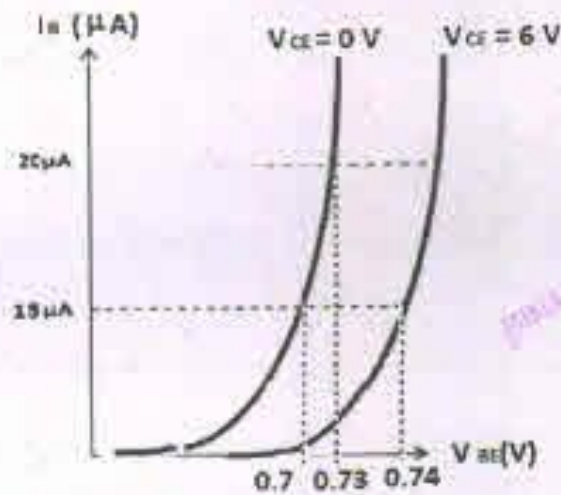2. (a) Derive the Shockley's Equation for current flow in a P-N Junction and justify the shape of the V-I Characteristics. (15)
- (b) (i) Calculate  $h_{ie}$  and  $h_{re}$  from the input characteristics of a transistor shown in the figure. All the required data are available in the sketch. (7)




- (ii) Sketch the DC Load line, locate the Q-Point and calculate the stability factor of a Voltage-Divider biasing circuit of a Si NPN transistor with the following component values:


$$R_C = 2 K, R_E = 1.5 K, R_1 = 15 K, R_2 = 2 K,$$

$$\text{Given, } \beta = 200, V_{CC} = +12 V \quad (8)$$

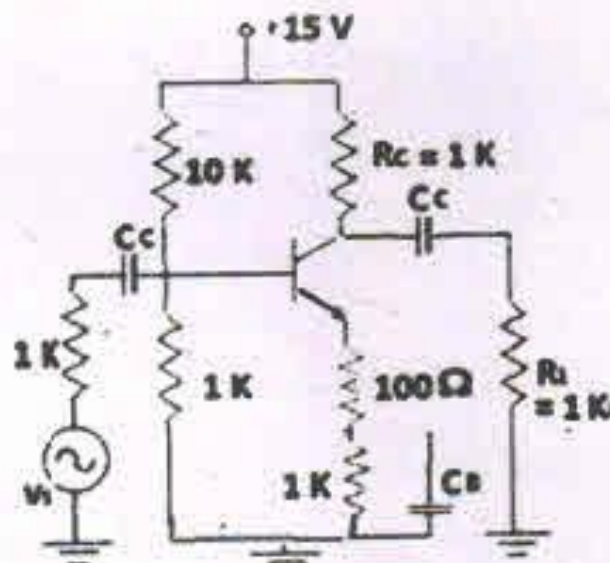3. (a) Calculate Voltage Gain, Current Gain, Input Impedance and Power gain of the amplifier circuit shown in the figure below using r-parameter analysis. The circuit uses a Si transistor having  $\beta = 200$ . (15)




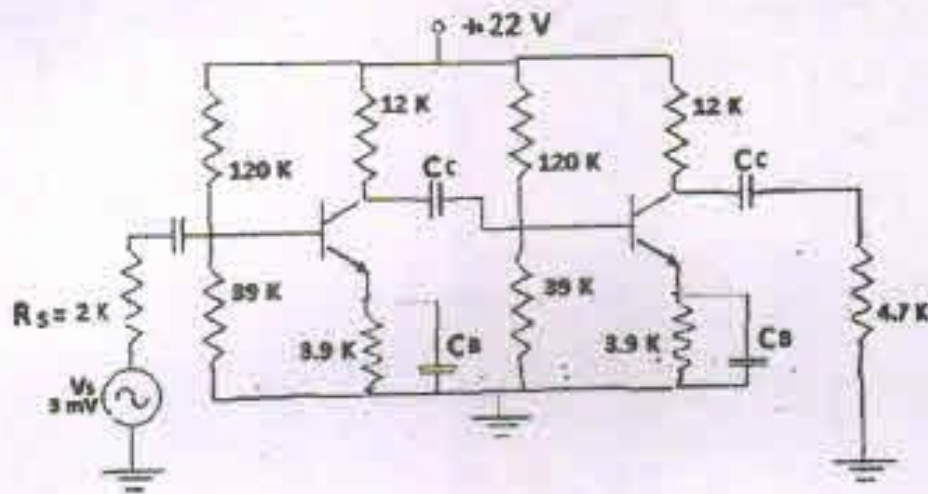- (b) Analyze the amplifier in the circuit shown in the figure below and calculate output voltage and output power. Assume identical transistors with  $h_{ie} = 2K$  and  $h_{fe} = 100$ . (15)



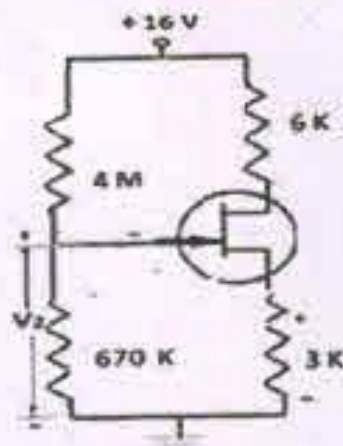4. (a) (i) An N-Channel JFET has the following parameters. Approximately sketch the Transfer Characteristics and Drain Characteristics of the CS Amplifier shown in the figure and locate the Q-Point.


Given,  $Y_{OS} = 40 \mu S$ ;  $I_{DSS} = 30 \text{ mA}$ ;  $V_p = 6V$ . (10)



BINA CHOWDURY CENTRAL LIBRARY  
II (M.T.S. & N.P.S.)  
2nd Floor, 1st Stage,  
Chowdury, 25017

- (ii) In a Voltage Series Negative Feedback system, the Basic Amplifier has a Voltage Gain of  $A_V = |40|$ , Input Impedance of  $3K$ , Output Impedance of  $100\Omega$  and a Bandwidth of  $20 \text{ KHz}$ . If the applied Feedback is 10% of the output, calculate following quantities for the system; (5)
- (1) Voltage Gain;
  - (2) Input Impedance;
  - (3) Output Impedance;
  - (4) Band-Width;
- (b) Explain in detail, the constructional features and the Working principle of a MOSFET which can be operated in both E-Mode and D-Mode. (15)

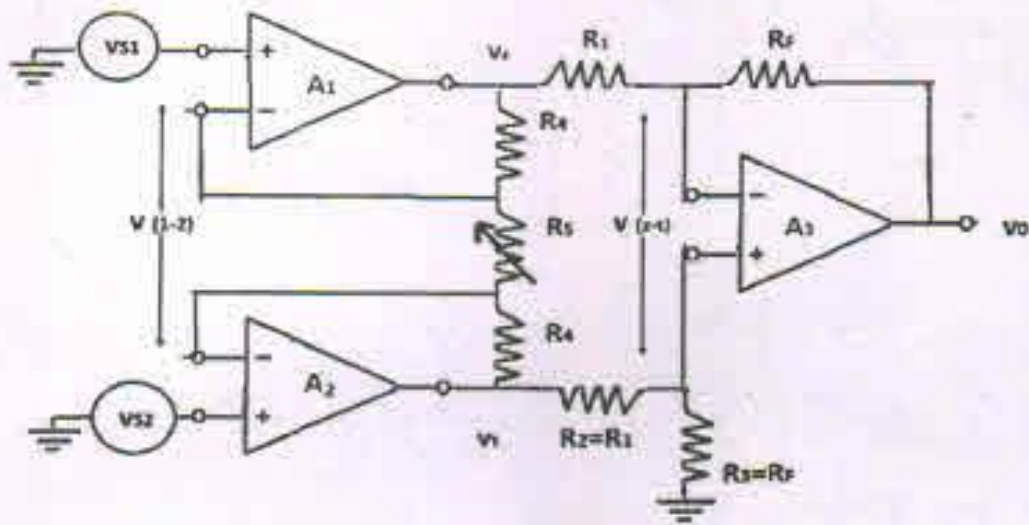5. (a) Show that the circuit shown in the figure below functions as a Difference Amplifier. Show that the Input Impedance at both the input terminals can be equalized. (15)



- (b) Design an OPAMP based application to simulate the given differential equation. (15)

$$2\ddot{y} - 14\dot{y} + 8y = 2u(t)$$

With the Initial conditions,

$$\dot{y}(0) = -12 ; y(0) = 6$$

BINA CHOWDHURY CENTRAL LIBRARY  
 2nd Floor  
 Anna University  
 Chennai - 600 025