

Total No. of printed pages = 6

EI 181302

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

22/2/22 2021

CHOWHURY CENTRAL LIBRARY
21/01/22 11:13 AM
3/2/22 11:13 AM
22/2/22 11:13 AM

B.Tech. 3rd Semester End-Term Examination

EE, IE, EEE

ELECTRICAL CIRCUIT ANALYSIS

(New Syllabus & New Regulation)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.


Answer question No. 1 and any *four* from the rest.

1. Answer the following (MCQ/ Fill in the blanks) : (10 × 1 = 10)
- (i) 'The algebraic sum of the powers in all branches of the network at any instant is zero' is valid when
- (a) The network obeys KCL
(b) The network obeys KVL
(c) The network obeys both KCL and KVL
(d) None of the above
- (ii) The coupling between two magnetically coupled coils is said to be ideal if the coefficient of coupling is
- (a) Zero (b) 2
(c) 1 (d) 0.5
- (iii) A resistance having rating 10 ohms, 10 W is likely to be a
- (a) Metallic resistor (b) Carbon resistor
(c) Wire wound resistor (d) Variable resistor


[Turn over

- (iv) In Thevenin's theorem applied to A.C. circuit, any linear network can be replaced by a voltage source
- In series with an impedance
 - In parallel with an impedance
 - In series with a resistance
 - In parallel with a resistance
- (v) The inductance of an iron-core coil decreases if
- The number of turns is decreased
 - The iron core is removed
 - The length of the coil decreases
 - None of the above
- (vi) The graph of an electrical network has n nodes and b branches. The number of links with respect to the choice of a tree is _____
- (vii) If the flux of two mutually coupled coils oppose each other then the equivalent inductance is given by
- $L = L_1 + L_2 + 2M$
 - $L = L_1 + L_2 - 2M$
 - $L = L_1 + L_2 + 4M$
 - $L = L_1 + L_2 - 4M$
- (viii) A two port network has transmission parameters A, B, C, D. The condition of reciprocity is
- $AC - BD = 1$
 - $AD - BC = 1$
 - $AB - DC = 1$
 - $BC - AD = 1$
- (ix) Which one of the following is true for an incidence matrix?
- Algebraic sum of the column entries of an incidence matrix is zero
 - Determinant of the incidence matrix of a closed loop is zero
 - Both the above statements are true
 - None of the above
- (x) For an R-C driving point impedance function, the poles and zeros
- should alternate on the real axis
 - should alternate on the negative real axis
 - should alternate on the imaginary axis
 - can lie anywhere on the left half-plane

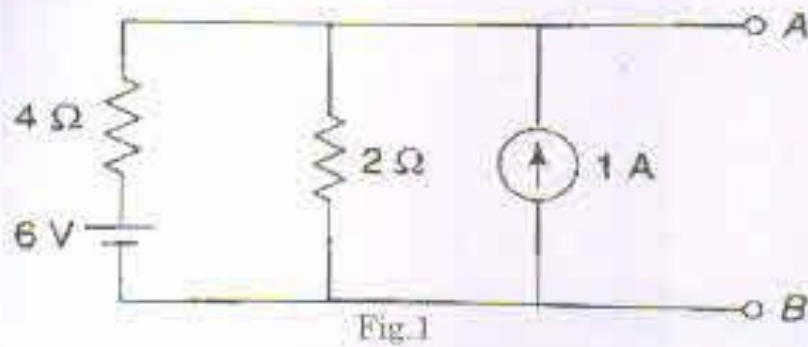
2. (a) Find the Millman's equivalent circuit for the circuit in Fig.1 on the left of the terminals A & B (4)



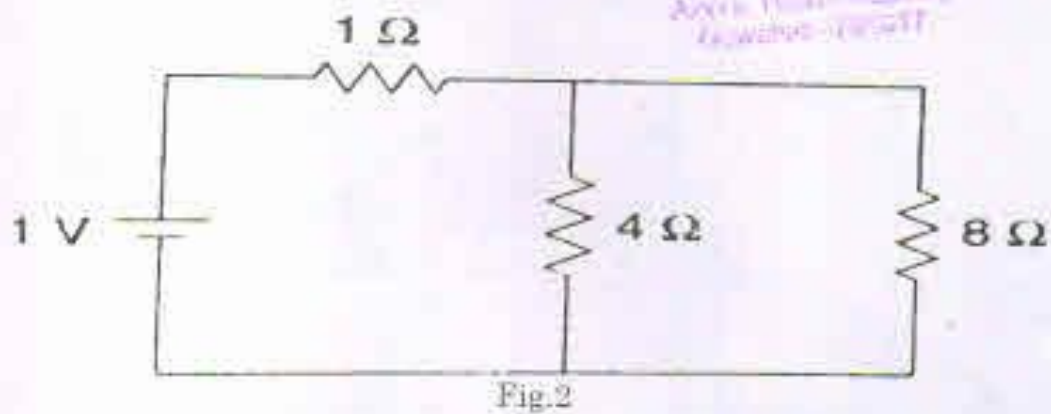- (b) In the network of Fig. 2 the resistance of 4 Ohm is changed to 2 Ohm. Verify the compensation theorem. (6)



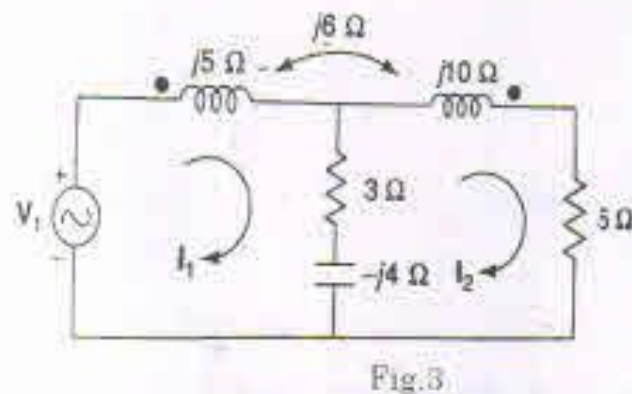- (c) Draw the conductively coupled equivalent circuit for the circuit of Fig.3 (5)



3. (a) The reduced incidence matrix of an oriented graph is (5)

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

- (i) Draw the oriented graph
 (ii) How many trees are possible for this graph?

- (b) The fundamental cut set matrix of a network is given as follows : (5)

Twigs			Links		
a	c	e	b	d	f
1	0	0	1	0	1
0	1	0	0	1	1
0	0	1	1	1	1

DINA CHANDRAN CENTRAL LIBRARY
 11/11/2019
 11:17 AM
 11/11/2019

Draw the oriented graph

- (c) For the graph shown in Fig.5, write the tie-set matrix and f -cut set matrix. (5)

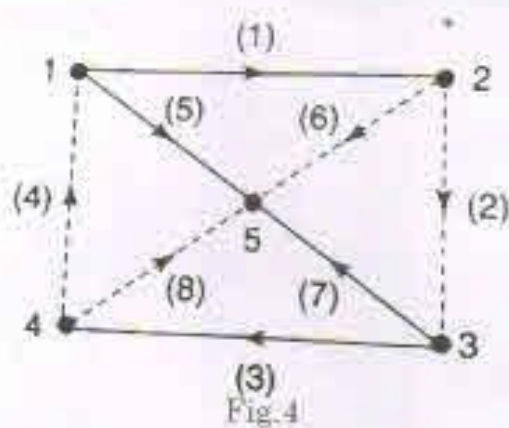


Fig.4

4. (a) In the two mesh network shown in Fig.5, find the currents which result when the switch is closed. (5)

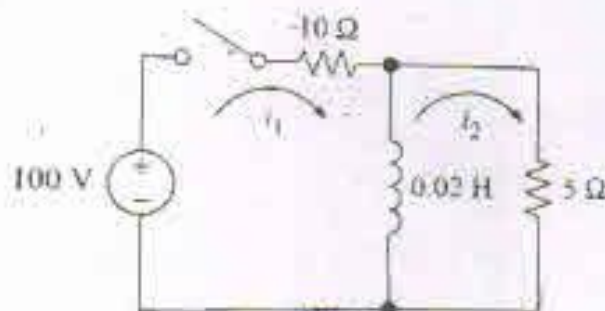


Fig.5

- (b) In the network shown in Fig.6, at $t = 0$, the switch is opened. Calculate v , dv/dt and d^2v/dt^2 at $t = 0$

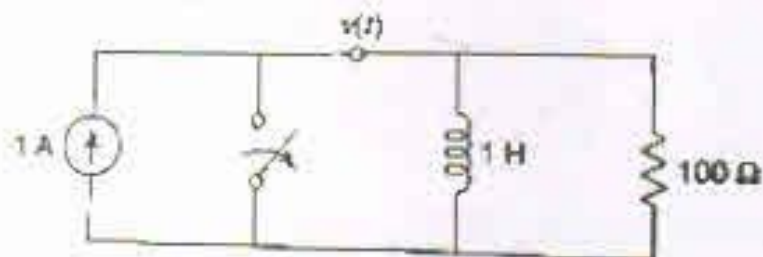


Fig.6

- (c) A parallel circuit comprises of two branches is excited by a current source of $10u(t)$ A through a switch. First branch is a resistance of 3Ω and the second is a resistance 2Ω in series with an inductance of 1 H. At $t=0$ sec the circuit is energized by closing the switch. After $t=0.5$ sec, the switch is opened again. Derive the expression of current in the circuit. And plot current Vs time.

5. (a) Derive the condition of reciprocity for ABCD parameters. (4)
- (b) Draw the h-parameter model of a 2-port network. Define the parameters with respective units and give the model equations. (5)
- (c) The following readings are obtained experimentally for an unknown two port network ; (6)

	V_1	V_2	I_1	I_2
Output open	100V	60 V	10A	0
Input open	30V	40V	0	3A

Compute the Z parameters. Also draw the Z parameter equivalent circuit for the above circuit.

6. (a) Determine the range of values of 'k' so that the polynomial $P(s) = s^3 + 3s^2 + 2s + k$ is Hurwitz? (5)
- WINA Group University, Uthmaniyah, Jordan
 J. Al-Mutairi & J. Al-Sayid
 Assoc. Prof. & Asst. Prof.
 E-mail: j-almutairi@winaj.edu.jo
- (b) Test whether $F(s) = (s^2 + 1) / (s^3 + 4s)$ is a positive real function? (5)
- (c) Realize the network having admittance function $Y(s) = (4s^2 + 6s) / (s + 1)$ (5)
7. (a) Compare the properties of different traditional and modern dielectric materials used in capacitors. (5)
- (b) Write short notes on the following : (3 × 2 = 6)
- (i) Metal film resistors
 - (ii) Tolerance and temperature stability of resistors
 - (iii) Properties of inductor core

(c) For the circuit shown Fig.7, obtain the branch currents

(4)

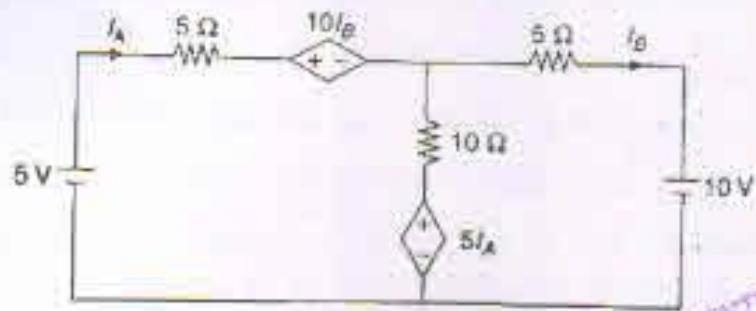


Fig.7

BNVA CHOUDHURY CENTRAL LIBRARY
PRINTED BY
BANKURA UNIVERSITY
BANKURA, WEST BENGAL