

Total No. of printed pages = 3

EI 181304

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

213722 2021

BNA UNIVERSITY
2021-22
K. J. Somaiya Institute of Technology
Mumbai - 400 072

B.Tech. 3rd Semester End-Term Examination

EE, EEE

ELECTRICAL MACHINES - I

(New Regulation and New Syllabus)

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks
for the questions.

I. Explain the followings:

[10 × 2 = 20]

- The shunt field winding of a d.c. machine consists of a large number of turns of thin wire while the series field winding consists of few turns of thick wire. Why?
- The armature of a d.c. machine is placed on the rotor and the field winding on the stator, and not otherwise, why?
- Why are equalizer connections necessary in lap wounded machine, but not in wave wounded machines?
- Why should a d.c. series motor not be started without some load on it?
- Why do we not get linear commutation in d.c. machine?
- Why does the terminal voltage of a d.c. shunt generator fall as the load on it is increased?
- Why and how does the primary of a transformer draw more current when the load on the secondary increases?
- Why, in transformer construction, the L.V. windings are placed near the core?
- Why, in the open circuit test of transformer, the instruments are placed on the L.V. side while in the short circuit test; these are placed on the H.V. side?
- Why should the turn-ratios of the transformers connected in parallel be same?

[Turn over

2. Answer any five:

(5 × 3 = 15)

- What is armature reaction? Describe, with suitable sketch(es), its effect on the operation of d.c. machines.
- Explain the fact that the parallel operation of d.c. shunt generators is inherently stable.
- Explain the necessity of starter in d.c. motors. What are the two protective features in 3-point starter? Describe their working. What is the essential difference between a 3-point starter and a 4-point starter?
- Draw and describe the 'armature current versus torque' and the 'armature current versus speed' characteristics of series, shunt and compound motors, and hence, comment on their applications.
- What is 'equivalent circuit' of a transformer, and how does it help in determining the performance of transformers? How are the parameters of the equivalent circuit determined?
- Derive an expression for saving of copper in an auto-transformer as compared to an equivalent two-winding transformer.
- What is open-delta connection of transformer? When is it employed? Derive the expression for kVA rating of such transformers in terms of normal delta-connected transformers.

BINA CHOWDHURY CENTRAL LIBRARY
2nd FLOOR
10/10/2020

3. Answer any FIVE:

(5 × 7 = 35)

- A 4-pole lap wound d.c. shunt generator supplies current of 143 A. The field current is 10 A. When delivering full-load, the brushes are given a lead of 10° (mech.). Find (i) the demagnetizing amp-turns, and (ii) the number of extra shunt field turns needed to neutralize the demagnetization.
- A 100-KW, belt-driven shunt generator running at 300 RPM on 220-V bus-bars continues to run as a motor when the belt breaks, then taking 10 kW. What will be its speed? Armature resistance = $0.025\ \Omega$; field resistance = $60\ \Omega$; contact drop due to each brush = 1 V. Ignore armature reaction.
- A 440-V D.C. shunt motor takes a current of 5.6 A on no-load and 68.3 A on full-load. Armature reaction weakens the field by 3% on full-load. Calculate the ratio of full-load speed to no-load speed. The armature and the field resistances are $0.18\ \Omega$ and $200\ \Omega$ respectively, and the total brush drop is 2V.
- Hopkinson's test on two identical d.c. machines gave the following test results:

Input voltage = 250 V, Input current = 10 A, Output current of generator = 60 A, Field current of generator = 4 A, Field current of motor = 3 A Armature resistance of each machine is $0.06\ \Omega$. Calculate the efficiencies of both the machines.

(e) The following data were obtained on a 4 KVA, 50 Hz, 230/460 V, single-phase transformer.

O.C. test (with H.V. side open circuited): 230V, 0.6 A, 75 W

S.C. test (with L.V. side short -circuited): 20 V, 10 A, 60 W

(i) Compute the parameters of the approximate equivalent circuit referred to the high voltage side.

(ii) Find the efficiency and the voltage at the secondary terminals when supplying full-load current at p.f. 0.8 lagging.

(f) Two single-phase transformers with equal voltage ratios have impedances $(0.819 + j2.503) \Omega$ and $(0.819 + j2.503) \Omega$ respectively as referred to their secondaries. If they operate in parallel to share a load of 2000 kW at 0.8 p.f. lagging, how will they share the load?

(g) A 400/100 V, 10 KVA 2-winding transformer is to be used as auto-transformer to supply a 400 V circuit from a 500 V source. When tested as a 2-winding transformer at rated load, and 0.85 p.f. lagging, its efficiency is found to be 0.97. Determine (i) its KVA rating as an auto-transformer, (ii) the efficiency as an auto-transformer.

BANK CHANDRAN CENTRAL LIBRARY
M.T.S. 2014
193