

Total No. of printed pages = 2

ECE 181303

Roll No. of candidate:

--	--	--	--	--	--	--	--	--	--

22/2 / 2021

B.E 3rd Semester End-Term Examination

ECE, ETE, PEIE

DIGITAL CIRCUITS

(New Regulation and New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer the following questions.

1. (a) Convert the followings: (2×2=4)
 - (i) $(129)_{10}$ into octal equivalent.
 - (ii) $(630.4)_9$ into binary equivalent.
- (b) Each of the following number is a signed binary number 01101, 10111 and 1101010. Determine the decimal value in each case, if they are in (3×2=6)
 - (i) Sign-magnitude form
 - (ii) 2's complement form
 - (iii) 1's complement form
2. (a) Define SOP and POS term. Convert the Boolean expression $\overline{A}BC + \overline{B}CD + A\overline{C}D$ to SOP form. (7)
- (b) Simply the Boolean expression using K-Map $f(A, B, C, D) = \sum m(1,5,6,12,13,14) + d(2,4)$ (8)
3. (a) What is the difference between combinational and sequential circuits? (2)
- (b) How latches are different from flip-flops? What is race around condition? How can it be eliminated? (2+2+3)
- (c) Design a T Flip-Flop using S-R Flip Flop. (6)

[Turn over

4. (a) What is difference between asynchronous and synchronous counters? How many flip-flops are required to construct a BCD counter? (2+1)
- (b) Design a Mod-5 ripple down counter using D-flip Flop. (7)
- (c) Draw the circuit diagram for serial-in parallel-out shift register. (5)
5. (a) Explain the working of TTL NAND gate with neat diagram. (4)
- (b) Design an inverter using CMOS logic. (3)
- (c) Write short note on any two; (2×4=8)
- (i) Moore and Mealy state machine.
- (ii) Ring Counter.
- (iii) Fan-in and Fan-out.
- (iv) FPGA.

BINA CHOWDURY CENTRAL LIBRARY
UNIT 5 (301)
2nd Floor, Haldia, Kolkata
Date: 17/11/2017