

Total No. of printed pages = 6

ECE 181302

Roll No. of candidate

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

BINA CHOWDHURY CENTRAL LIBRARY
JALPAIGURI UNIVERSITY
JALPAIGURI
25/12/2021

25/12/22 2021

B.Tech. 3rd Semester End-Term Examination

ECE, ETE, PEIE, EEE

SEMICONDUCTOR DEVICES AND CIRCUITS

(New Regulation & New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer question No. 1 and any *four* from the rest.

I. Answer the following questions (MCQ/ Fill in the blanks): (10 × 1 = 10)

(i) When we decrease the doping level of the pn diode, the junction breakdown voltage will

- (a) increase (b) decrease
(c) become zero (d) have no impact

(ii) A pn diode is a _____

- (a) voltage-controlled resistance
(b) unidirectional switch
(c) bidirectional switch
(d) amplifier

(iii) We have a special purpose diode used for voltage-controlled-capacitance. It is a _____

- (a) Zener diode (b) LED
(c) Photo diode (d) Varactor diode

[Turn over

- (iv) _____ causes tunnelling effect in tunnel diodes.
- (v) In a BJT most of the majority carriers from the emitter
- Recombine in the base
 - Recombine in the emitter
 - Pass through the base region to the collector
 - None is correct
- (vi) The quiescent point is the _____
- Load line
 - KVL
 - Transfer characteristic
 - Intersection point of the network equation and device characteristic
- (vii) The transistor in a circuit is biased in order to ensure a _____
- proper direct current
 - proper alternating current
 - small base current
 - large collector current
- (viii) An ac signal applied to the BJT amplifier will move the operating point along the
- dc load line
 - ac load line
 - dc load line and ac load line
 - Ic axis
- (ix) The ac drain resistance of the JFET is
- $\frac{\Delta V_{DS}}{\Delta I_D}$ at constant I_{GS}
 - $\frac{\Delta V_{GS}}{\Delta I_D}$ at constant I_{DS}
 - $\frac{\Delta V_{DS}}{\Delta I_{GS}}$ at constant I_{DS}
 - $\frac{\Delta I_D}{\Delta V_{DS}}$ at constant I_{GS}

BINA CHOWDHURY CENTRAL LIBRARY
 KOLKATA
 2024 FEB 12 11:17 AM
 91-70402-7912-17

(x) A transistor can be used as a switch in the

- (a) active region
- (b) cutoff region
- (c) saturation regions
- (d) cutoff region and saturation regions.

PINA CHOWDHURY CENTRAL LIBRARY
UNIT 4 PPSY
K. J. Somaiya Institute of Technology
Mumbai - 400 072

2. (a) Two diodes with saturation currents I_{S1} and I_{S2} are connected in parallel with their cathodes joined together and connected to grounds. The two anodes are joined together and fed with a constant current I . Find the currents I_{D1} and I_{D2} that flow through the two diodes, and the voltage V_D that appears across their parallel combination.

(b) A junction diode is operated in a circuit in which it is supplied with a constant current I . What is the effect on the forward voltage of the diode if an identical diode is connected in (5)

- (i) series
- (ii) parallel

3. (a) In Figure 1 cut-in voltage of diode $D1$ is 0.7 V and that of diode $D2$ is 6.5 V . If the input voltage $V_I = 10\text{ V}$, determine the value of R_1 when the value of $I_{D2} = 2I_{D1}$. Also find the values of V_O , I_{D1} , and I_{D2} . Assume that all diodes are forward-biased. (10)

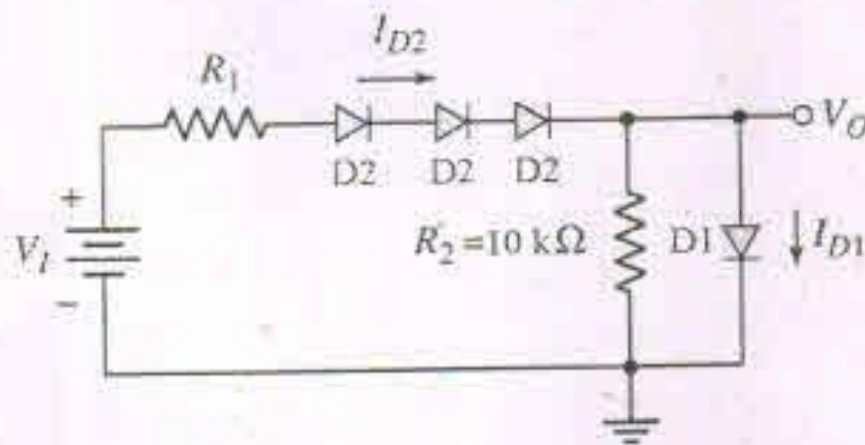


Figure 1

(b) Illustrate the difference between dc load line and ac load line. (5)

4. (a) Determine the output voltage waveform for the diode limiter shown in Figure 2. (8)

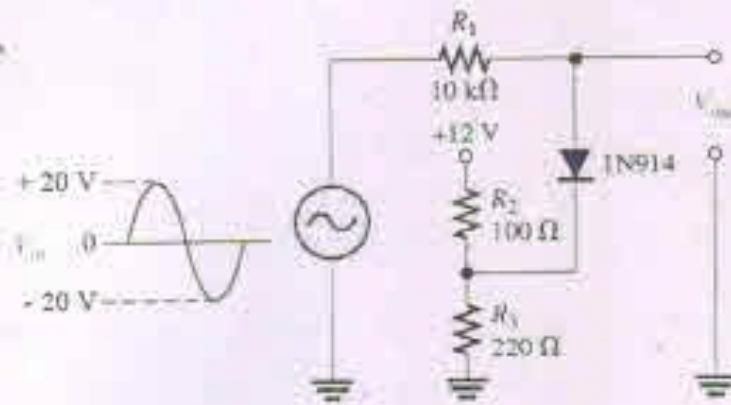


Figure 2

- (b) Two 10V Zener diodes are used in the voltage regulator in Figure 3. The input voltage varies between 10 V and 20 V while the load current varies between 12 mA and 8 mA. The minimum Zener current is 15 mA. Find the value of the variable load R_L . (7)

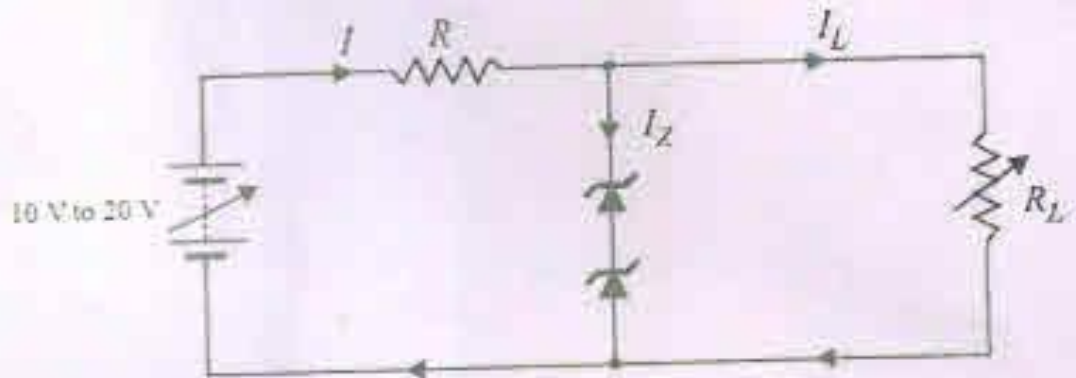


Figure 3.

5. (a) Determine (i) I_i (ii) Z_i (iii) V_o (iv) I_o (v) A_i (vi) V_o for the BJT amplifier in Figure 4. (10)

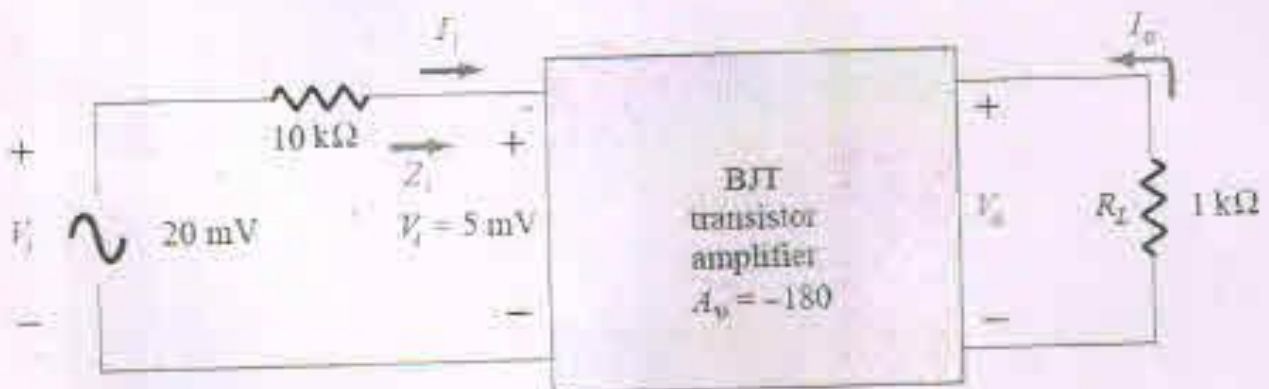


Figure 4

- (b) The output (collector voltage) of a biased transistor amplifier is shown in Figure 5. Is the transistor biased too close to cutoff or too close to saturation? (5)

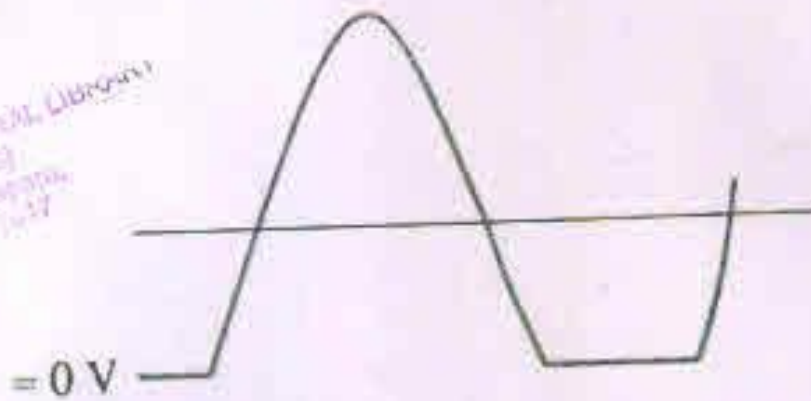


Figure 5

6. (a) Determine A_v and A_i for the network of Figure 6. (10)

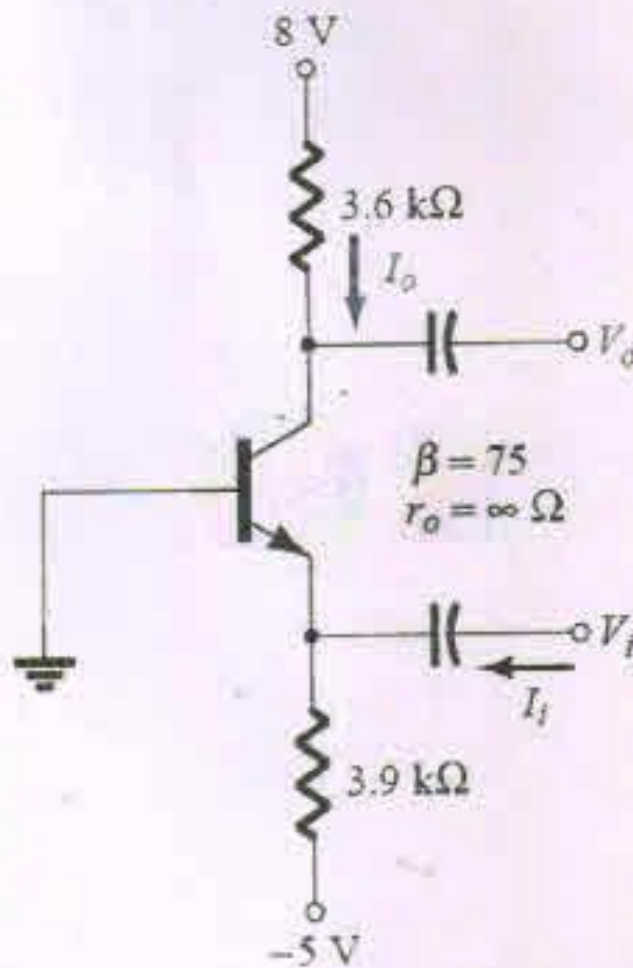


Figure 6

(b) Determine V_{GSQ} and I_{DQ} , V_D and V_C for the network in Figure 7.

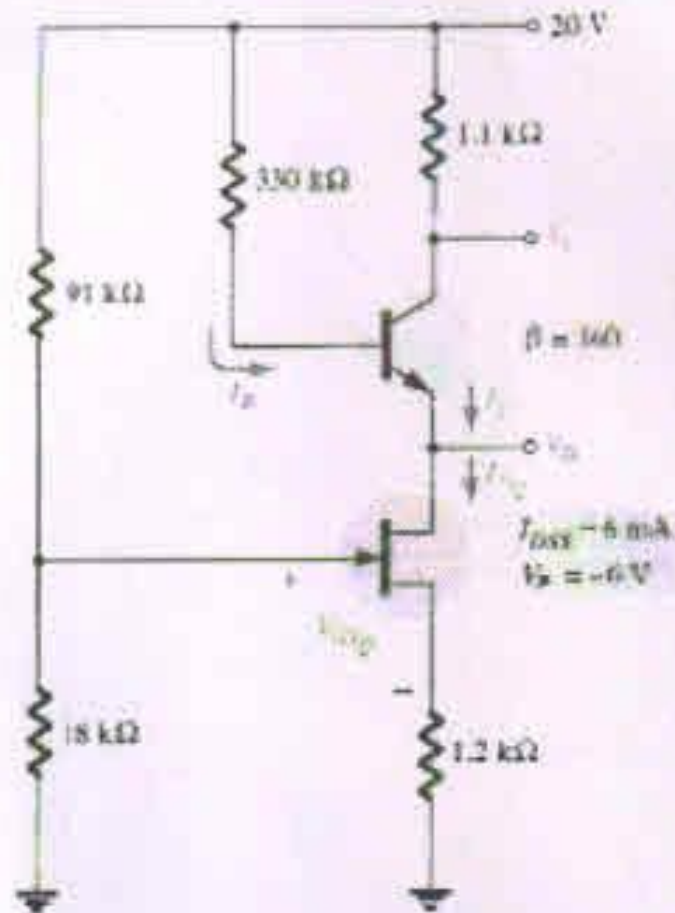


Figure 7.

7. Write short notes on (any three) :

(15)

- (a) MOSFET
- (b) Ebers-Moll Model
- (c) Hybrid equivalent model
- (d) Bridge rectifier.

BINA CHOWDHURY CENTRAL LIBRARY
 KJMT & JPS
 2017-18
 27/11/17