

Total No. of printed pages = 6

EC 131305

24/1/19

Roll No. of candidate

BINA CHOWDHURY CENTRAL LIBRARY (GIMT & GIPS) Azara, Hatkhowapara, Guwahati -781017									
---	--	--	--	--	--	--	--	--	--

2019

B.Tech. (ECE) 3rd Semester End-Term Examination

**ELECTRONIC MEASUREMENT AND
INSTRUMENTATION**

(New Regulation)

(w.e.f. 2017-2018)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer Q.No. 1 and any *four* from the rest.

1. Choose the correct answer for the following multiple
choice question: (10 × 1 = 10)

(i) Schering bridge is used to measure:

- (a) Capacitance (b) Resistance
(c) Inductance (d) None of these

(ii) When the feedback resistor connecting the
inverting and output terminal is set to zero,
then the output will be the _____
version of the input in the non inverting end of
the op-amp.

- (a) same (b) amplified
(c) attenuated (d) none of the above

[Turn over

(iii) A moving iron instrument is used as an ammeter, its range can be extended by using:

- (a) Suitable shunt across its terminal
- (b) A high inductive resistance
- (c) Either (a) or (b)
- (d) Neither (a) nor (b)

(iv) A moving system in the indicating instrument is subjected to:

- (a) Deflecting torque (b) Controlling torque
- (c) Damping torque (d) All the above

(v) A null type of bridge with DC excitation is commonly known as:

- (a) Wheatstone bridge
- (b) Anderson bridge
- (c) Hay's bridge
- (d) Schering bridge

(vi) Under balanced condition, the current flowing through the detector is equal to:

- (a) 1A
- (b) 0A
- (c) Sum of the current flowing in the adjacent arm
- (d) Difference between the current flowing in the adjacent arm

d) A basic D'Arsonval galvanometer movement with $R_m = 100 \Omega$ and full scale deflection current $I_{fsd} = 1 \text{ mA}$ is to be converted into a multi range DC voltmeter with voltage ranges:

- (i) 0-10 V
- (ii) 0-250 V
- (iii) 0-500 V.

Draw the necessary circuit arrangement and find the value of the suitable multipliers. (2 + 3 + 5 + 5 = 15)

3. (a) Compare Hay's bridge and Maxwell's bridge.
- (b) Derive the expression for bridge sensitivity for a Wheatstone bridge with equal arm.
- (c) An ac bridge has the following constants: arm ab : a capacitor C_1 in series with a resistance r_1 , arm bc : $R_3 = 2000 \Omega$, arm cd : $R_4 = 2850 \Omega$, arm da : $C_2 = 0.5 \mu\text{F}$ in series with $r_2 = 0.4 \Omega$ and $R_2 = 4.8 \Omega$. A supply of 450 Hz is given between 'a' and 'c' and the detector is connected between 'b' and 'd'. Calculate the value of the constants of arm ab and also find the dissipation factor for the capacitor. (3 + 4 + 8 = 15)

4. (a) What are ideal op-amp characteristics?
(b) Derive the relation of output voltage of an op-amp in terms of CMRR as given

$$V_{out} = A_d V_d [1 + (1/CMRR)(V_{cm}/V_d)]$$

where, V_{out} = output voltage

A_d = differential gain

V_d = differential voltage

V_{cm} = common mode voltage.

- (c) Sketch the circuit of a summing amplifier to get an output voltage $V_0 = -V_1 + 2V_2 - 3V_3$.
- (d) The 741 C is used as an inverting amplifier with a gain of 50. The sinusoidal input has a variable frequency and the maximum amplitude of 20 mV peak. What is the maximum frequency of the input at which the output is undistorted? (3 + 3 + 4 + 5 = 15)
5. (a) Quantization is done before sampling in A/D conversion process. (True/False). Justify your answer.
- (b) Explain the operation of sample and hold circuit with a neat diagram.
- (c) For a 5 bit R-2R ladder DAC, calculate the analog output voltage when the input is:
(i) 00001 (ii) 10000 (iii) 11111
Given, $R_F = 5 \text{ k}\Omega$, $R = 5 \text{ k}\Omega$, $V_{ref} = 10 \text{ V}$.
- (d) Describe the operation of ramp type ADC with a suitable diagram. (3 + 3 + 4 + 5 = 15)

6. (a) What are rise time, fall time and delay time in CRO?
- (b) For the given Lissajous pattern, find the frequency of the vertical signal if the frequency of the horizontal signal is 3 kHz.



- (c) How oscilloscope can be used to measure voltage, current, frequency and phase?
- (d) Explain the deflection mechanism used in CRO.
(3 + 3 + 4 + 5 = 15)
7. Write short note on any *three* of the following :
(3 × 5 = 15)
- (a) Digital voltmeter.
- (b) Comparison between analog and digital multimeter.
- (c) Frequency meter.
- (d) Ohm meter.
- (e) Owen's bridge.