

Total No. of printed pages = 3

BINA CHOWDHURY CENTRAL LIBRARY

(GIMT & GIPS)

Azara, Hatkhowapara

Guwahati - 781017

EC 131701 NR

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--

8/2/2021

B.Tech. 7<sup>th</sup> Semester End-Term Examination

ECE + AEI

LINEAR INTEGRATED CIRCUITS

(New Regulation)

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks  
for the questions.

GROUP - A

1. Answer *all* the question : (10)
- If one of the input and output of an ideal op-amp is 2V and 12V and the gain is 3, then the other input of the ideal op-amp is (8V / 4V / -4V / -2V)
  - (Infinite voltage gain / Infinite bandwidth / Infinite output resistance / Infinite slew rate) is not the ideal characteristic of an op-amp.
  - In ideal Differential amplifier, if same signal is given to both inputs, then output will be (same as input / double the input / Not equal to zero / zero)
  - Level shifter in op-amp internal circuit is to (Adjust DC voltage / Increased impedance / Provide high gain / Decrease input resistance)
  - CMRR of a differential amplifier can be improved by decreasing (Differential voltage gain / Common mode voltage gain / Both / None of these)
  - An inverting amplifier with gain of 1 have different input voltage 1.5V, 2.4V and 3.6V. The output voltage will be ( 3.9V / 7.5V / -7.5V / -3.9V)
  - For an ideal comparator the value of the response time is (Zero / Unity / Infinite / unpredictable)

[Turn over

- (viii) The feedback factor of voltage follower circuit is (zero / unity / Infinity / Between zero and one)
- (ix) (V to I converter / Comparator / Precision rectifier / Instrumentation amplifier) is a non linear application of op-amp.
- (x) In an inverting ideal differentiator (R /L / C /Diode) is present in the feedback path.

GROUP – B

BINA CHOWDHURY CENTRAL LIBRARY  
3 (BMIT & BIPS)  
42/112, Hathi, Gopara,  
Bhowahat, 751017

Answer any four questions.

2. (a) Derive  $A_v$ ,  $R_i$ ,  $R_o$ , BW for an inverting mode negative feedback amplifier with a 741 OpAmp having  $R_1 = 1 \text{ K ohm}$  and  $R_f = 40 \text{ K ohm}$ . (6)
- (b) Draw the internal block diagram of Op-Amp. Explain each block. (6)
- (c) Explain the significance of virtual ground in an op-amp. (3)
3. (a) What is input and output offset? How are they compensated? (5)
- (b) With a neat circuit diagram explain the working of voltage to current converter. (6)
- (c) Define Slew rate. An operational amplifier has a slew rate of  $4\text{v}/\mu\text{s}$ . Determine the maximum frequency of operation to produce distortion less output swing of  $12\text{V}$ . (4)
4. (a) Draw the schematic of a linear IC triangular waveform generator and explain the circuit operation. (8)
- (b) Draw the circuit diagram of a comparator. Mention its application. (7)
5. (a) Explain the operation of the following circuits (10)
- (i) Zero cross detector
- (ii) Clipper and clamper circuit.
- (b) Describe the process of hysteresis generation in Schmitt trigger circuit. (5)
6. (a) With a neat circuit diagram explain the working of linear voltage regulator using operational amplifier. (6)
- (b) Design a second order low pass filter using operational amplifier for the upper cut off frequency of  $2 \text{ KHz}$ . Assume the value of the capacitor to be  $0.1 \mu\text{F}$ . (6)
- (c) Define Capture range and Lock range of PLL. (3)

7. (a) Describe the 555 Timer IC. Design a Astable Multivibrator Circuit to generate output Pulses of 50% duty cycle using 555 Timer IC, with  $C = 0.01 \mu\text{F}$ , Frequency as 4 KHz. (10)
- (b) Calculate the value of the LSB, MSB, and full scale output for an 8-bit DAC for the 0 to 12V range. (5)

MINA CHOWDHURY CENTRAL LIBRARY  
(B.M.T & TIPS)  
57-2 Hatki Wapam  
Waher P.O.