

Total No. of printed pages = 6

ECE 181304

Roll No. of candidate

17/12/23

--	--	--	--	--	--	--	--	--	--

2023

BINA CHOWDHURY CENTRAL LIBRARY
(GIMT & GIPS)
Azara, Hatikhowapara,
Guwahati - 781017

B.Tech. 3rd Semester End-Term Examination

ETE / ECE

NETWORK THEORY

(New Regulation and New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer Question No. 1 and any *four* from the rest.

1. Choose the correct answer : (10 × 1 = 10)
- (i) A network which contains one or more than one source of emf is known as
- (a) Linear network (b) Non linear network
- (c) Passive network (d) Active network
- (ii) A non-linear network does not satisfy
- (a) Superposition condition
- (b) Homogeneity condition
- (c) Both Homogeneity and Superposition condition
- (d) Homogeneity, Superposition and associative condition
- (iii) The no. of independent equations to solve a network is equal to _____.
- (a) The number of chords
- (b) The number of branches
- (c) Sum of the no of branches and chords
- (d) Sum of the no of branches, chords and nodes

[Turn over

(iv) For determining the polarity of a voltage drop across a resistor, it is necessary to know the

- (a) Value of resistor
(b) Value of current
(c) Direction of current flowing through the resistor
(d) Value of emf in the circuit

BINA CHOWDHURY CENTRAL LIBRARY
(CMT & GIPS)
Azara, Hatkhowanpara,
Guwahati - 781017

(v) What is the condition on Z-parameters for a reciprocal network

- (a) $z_{11} = z_{22}$
(b) $z_{12} = z_{21}$
(c) $z_{12} = z_{11}$
(d) $z_{22} = z_{21}$

(vi) The cut-off frequency of a series RL low-pass filter is

- (a) $W_c = \frac{L}{R}$
(b) $W_c = \frac{R}{L}$
(c) $W_c = \frac{1}{LR}$
(d) $W_c = LR$

(vii) The rms value of a sine wave is 100 A. Its peak value is

- (a) 131.4 A
(b) 141.4 A
(c) 151.4 A
(d) 161.4 A

(viii) The ratio of active power to apparent power is known as

- (a) RMS value
(b) Peak factor
(c) Power factor
(d) Form factor


(ix) What is the dual of charge?

- (a) Resistor
(b) Capacitor
(c) Inductor
(d) Flux


(x) A delta circuit has each element of value $R/2$. The equivalent elements of the star circuit will be

- (a) $R/6$
(b) $R/3$
(c) $2R$
(d) $3R$

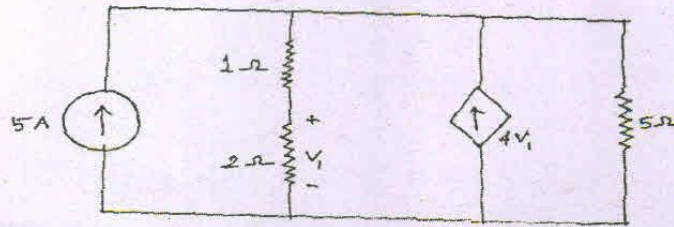
2. (a) Find the power absorbed by the 5Ω resistor. (5)




- (b) Find v_0 and i_0 . (4)

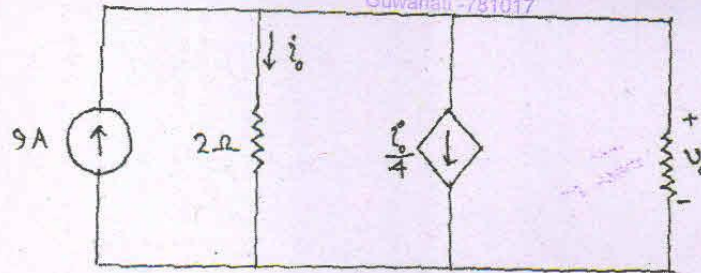

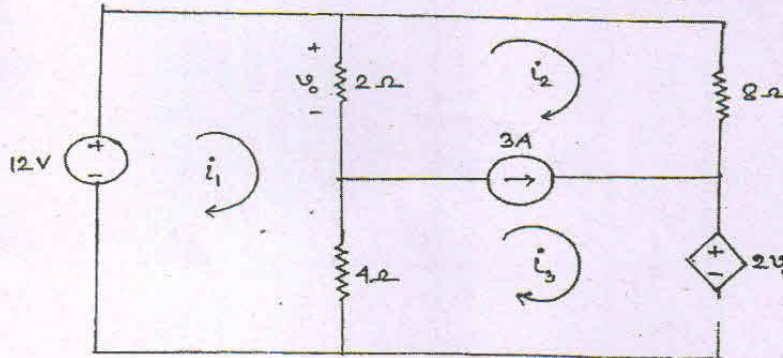
- (c) Find i_1 , i_2 and i_3 in the circuit below: (6)



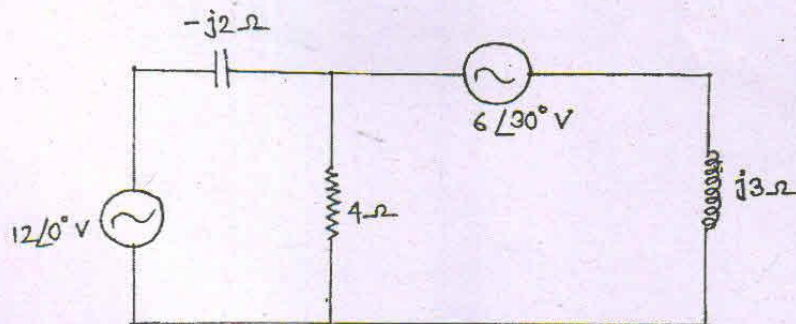
3. (a) Find the current through $j3\Omega$. (7)



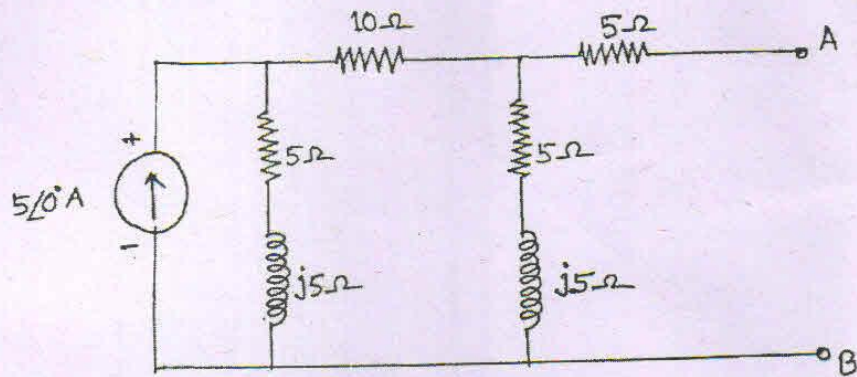
- (b) Find the value of Z_L to be connected between the terminals AB for maximum power transfer. Find maximum power. (8)



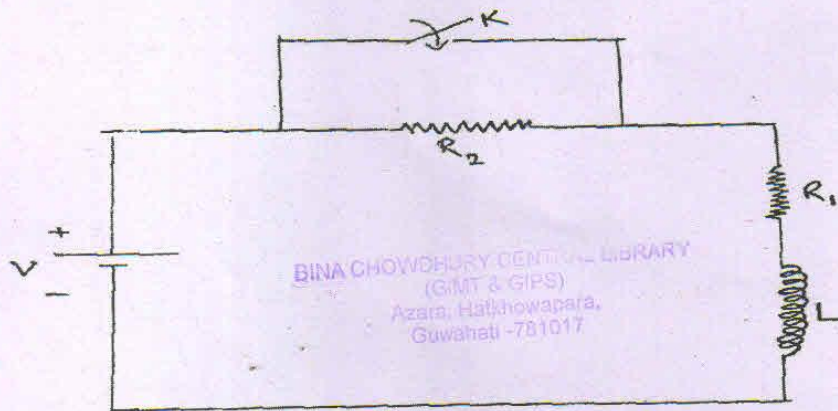
4. (a) Find $i(t)$ in the circuit when the switch 'K' closed at $t=0$. (8)



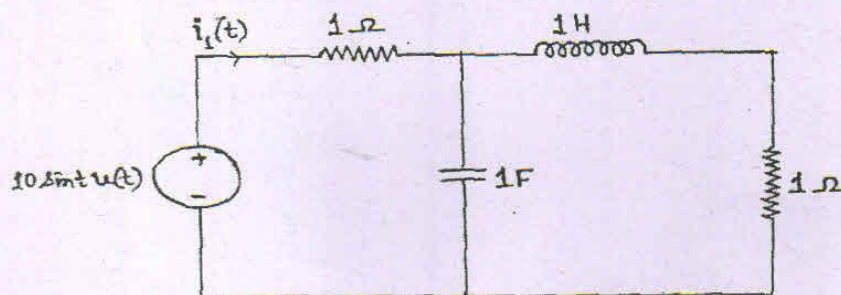
- (b) Find $I_1(s)$. Assume all initial conditions to zero. (7)



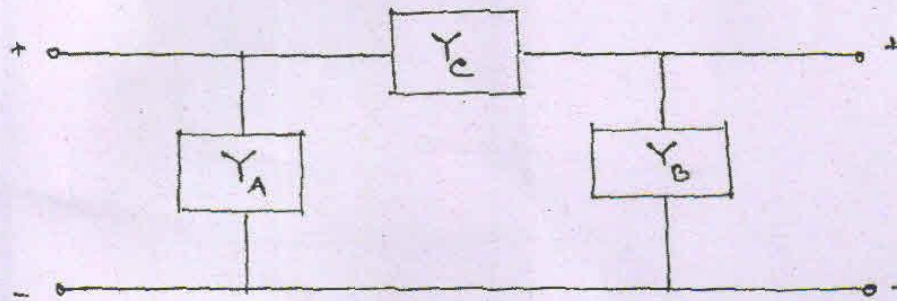
5. (a) Through Derivation express Z -parameters in terms of Y -parameters. (5)
 (b) Find Y -parameters of the network. (5)



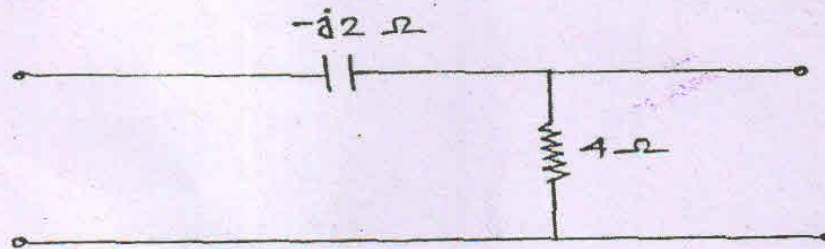- (c) Find the transmission parameters for the circuit. (5)




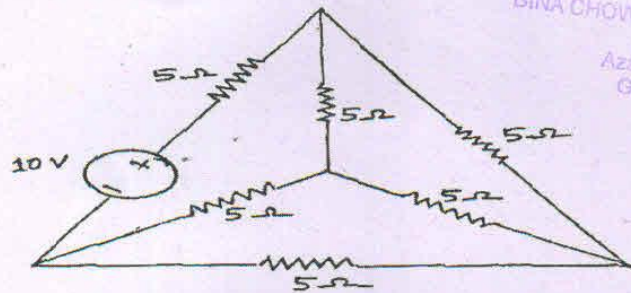6. (a) Draw the graph of the network below. Find incidence matrix and f-cutset matrix. (10)




BINA CHOWDHURY CENTRAL LIBRARY
 (GIMT & GIPS)
 Azara, Hatkhowapara,
 Guwahati -781017

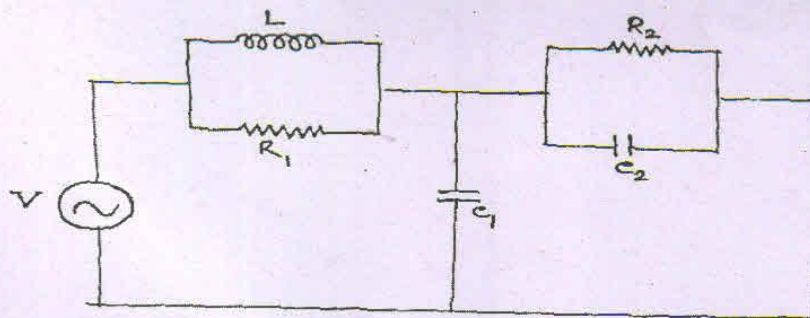- (b) Construct the dual of the network. (5)



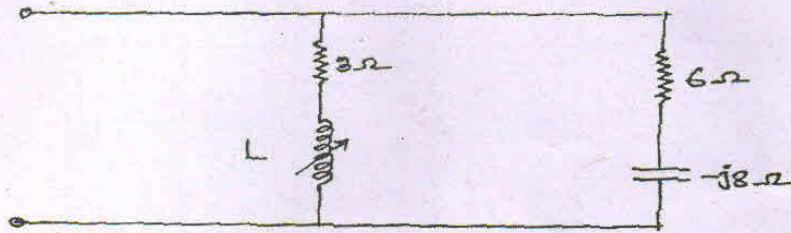7. (a) Find the value of L for which the circuit is resonant at a frequency $\omega = 10000$ rad/sec. (5)



- (b) Define passive filter. Explain different types of passive filters with proper diagram. (5)
- (c) Find the power dissipated in $1\ \Omega$ resistor. (5)

BINA CHOWDHURY CENTRAL LIBRARY
(GIMT & GIPS)
Azara, Heikhowapara,
Guwahati - 781017

