

Total No. of printed pages = 3

ECE 181402

Roll No. of candidate

170122

--	--	--	--	--	--	--	--	--	--

2022

BINA CHOWDHURY (GATE & GATE)
Azara, Haldighatpara,
Guwahati - 781017

B.Tech. 4th Semester End-Term Examination

ANALOG CIRCUITS

(New Regulation & New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer question No. 1 and any *four* from the rest.

1. Answer the following : (10 × 1 = 10)
- (i) The f_a is proportional to the cut off frequency at which the common-emitter short circuit small signal forward current transfer ratio A_f has dropped by 3dB from its value at low frequency
- (a) True (b) False
- (ii) Du a voltage series feedback amplifier _____
- (a) The input impedance increases but the output impedance decreases
- (b) Both input and output impedance increases
- (c) Both input and output impedance decrease
- (d) The input impedance decreases but the output impedance increases
- (iii) Du a crystal oscillator the crystal is equivalent to a
- (a) Tuned circuit with high Q
- (b) Tuned circuit with low Q
- (c) Any RC circuit
- (d) Any RL circuit
- (iv) The lower cut of frequency of a two stage RC coupled amplifier is
- (a) Higher than its value for the single stage amplifier
- (b) Lower than its value for the single stage amplifier
- (c) Equivalent to its value for the single stage amplifier
- (d) It random

[Turn over

- (v) When SCR is conducting, the anode terminal of the SCR is always
- At positive potential with respect to the cathode
 - At negative potential with respect to the cathode
 - At zero
 - At the same potential with the cathode
- (vi) Du a class B push-pull amplifier
- The transistor is biased at saturation region
 - The transistor is biased at cut of near cut off region
 - The transistor is biased at active region
 - The transistor is left open
- (vii) The voltage that starts an oscillator is caused by the noise voltage in resistor
- True
 - False
- (viii) Du a CE amplifier, the lower cut off frequency is Decided by
- The emitter bypass capacitor
 - The coupling capacitor
 - The load
 - The base current
- (ix) Du a class and amplifier
- Current flows for half of the entire cycle
 - Current flows for the entire cycle
 - Current flows for less than half of the entire cycle
 - Current flows for more than half of the cycle but less than the entire cycle
- (x) Du a negative feedback amplifier circuit
- The gain can be controlled
 - The gain is infinite
 - The gain is zero
 - The gain is unity

BINA CHOWDHURY CENTRAL LIBRARY -
(CMT & GIPS)
Azara, Halkhowapara,
Guwahati - 781017

2. (a) What is a trans-conductance amplifier. (2)
- (b) Discuss the working principle of a current mirror circuit. What is the need of the circuit. (8)
- (c) Derive the voltage gain of a common base amplifier circuit. (5)

3. (a) (i) Draw a circuit diagram of a two-stage RC coupled BJT amplifier. Draw the frequency response of an RC coupled amplifier. (2+2)
- (ii) What is direct coupled amplifier? Write applications of a direct coupled amplifier. (2)
- (b) (i) Draw the circuit diagram of a class A amplifier and explain its operation briefly. (2+3)
- (ii) Derive the equation for efficiency of a class A amplifier. (4)
4. (a) (i) In a voltage- series feedback amplifier $A=400$, $R_i=3\text{ K}\Omega$, $R_o=100\text{ K}\Omega$ and $\beta=0.1$. Determine overall gain, input impedance, and output impedance of feedback amplifier. (3)
- (ii) Calculate the overall loop gain, input and output impedances for an amplifier in a current series feedback amplifier with $A=100$, $R_i=10\text{ K}\Omega$, $R_o=50\text{ K}\Omega$ and $\beta=0.025$. (2)
- (b) A class B push-pull power amplifier is supplied with $V_{cc}=50\text{ V}$. The signal swings the collector voltage down to V_{min} of 5V . The total dissipation in both transistor is 40 W . Find the
- (i) Total power (ii) Conversion efficiency (5+5=10)
5. (a) Draw the circuit diagram of a differential amplifier and derive the gain of the circuit. What are the advantages of a differential amplifier over single stage (10)
- (b) What is CMRR? Discuss its significance. (5)
6. (a) An R-C coupled amplifier has mid-frequency gain of 200 and a frequency response from 100 Hz to 20 kHz . A negative feedback network with $\beta=0.2$ is incorporated into the amplifier circuit. Find the bandwidth after feedback. (4)
- (b) What is Barkhausen criterion? Explain the working of Hartley oscillator with neat diagram. (5)
- (c) In a Hartley oscillator circuit $C=500\text{ pf}$, $L_1=20\text{ mH}$ and $L_2=5\text{ mH}$. Find
- (i) frequency of oscillation
- (ii) sketch Hartley oscillator circuit using BJT. (6)
7. (a) List three advantages and disadvantages of active filter over passive filters. (3)
- (b) List the characteristics of an ideal OPAMP. (4)
- (c) Describe a log amplifier using OPAMP and show the output is proportional to logarithm of the input voltage. (8)