

Total No. of printed pages = 3

ECE 181407

Roll No. of candidate

28/7/24

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

2022

SWINBURNE UNIVERSITY OF TECHNOLOGY
LIBRARY
(CIT 181407)
Azara, Hatibowapara,
Guwahati - 781017

B.Tech. 4th Semester End-Term Examination

APPLIED ELECTRONICS

(New Regulation & New Syllabus)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer Question No. 1 and any *four* from the rest.

1. Answer the following : (10 × 1 = 10)
- (i) An intrinsic semiconductor at the absolute zero temperature
- (a) behaves like an insulator (b) has large number of holes
(c) has large number of electrons (d) behaves like conductor
- (ii) Electron-hole pairs are produced by
- (a) doping (b) thermal energy
(c) ionization (d) Both (a) and (b)
- (iii) The cut in voltage of a Silicon diode is
- (a) 0.2 V (b) 0.6 V
(c) 0.8 V (d) 1.0 V
- (iv) A transistor has an α of 0.975. The value of β is
- (a) 43 (b) 39
(c) 0.995 (d) 80
- (v) A photodiode is a two terminal PN junction operates in
- (a) reverse bias
(b) forward bias
(c) both forward and reverse bias
(d) None of the above

[Turn over

(vi) A digital circuit that can store only one bit is called

- (a) register (b) memory
(c) flip-flop (d) NOR gate

(vii) An XOR function is expressed as

- (a) $\overline{AB} + AB$ (b) $\overline{A}B + A\overline{B}$
(c) $(\overline{A} + B)(A + \overline{B})$ (d) $(\overline{A} + \overline{B})(A + B)$

(viii) The robot designed with polar coordinate system has

- (a) three linear movements
(b) three rotational movements
(c) two linear and one rotational movement
(d) two rotational and one linear movement

(ix) Tachogenerator is used to measure

- (a) force
(b) displacement
(c) angular velocity of a rotating shaft
(d) temperature

(x) The number of moveable joints in the base, the arm and the end effectors of the robot determines

- (a) flexibility (b) payload capacity
(c) degree of freedom (d) None of the above

2. (a) Differentiate between N-type and P-type semiconductor materials. Name three acceptor and three donor materials for doping of a semiconductor.

(3 + 2 = 5)

(b) Explain the generation of holes and electrons in an intrinsic semiconductor. (5)

(c) Discuss the process of formation of depletion layer at PN junction. (5)

3. (a) Explain the two-breakdown mechanism of a reverse biased diode. (6)

(b) Draw the circuit symbol and also draw the V-I characteristics of a PN junction diode when it is (i) forward biased and (ii) reverse biased.

(1 + 5 = 6)

- (c) Determine the range of supply voltage that will maintain Zener diode in break-down state i.e $V_z = 10$ v. Assume R (series resistance) = 330Ω , $R_L = 1 K\Omega$ and maximum allowable Zener current $I_{zmax} = 20$ mA. (3)
4. (a) Illustrate with necessary figures, explain the principle of operation of a PNP transistor. (6)
- (b) What is Q point? Draw the circuit diagram of an inverting amplifier. Also derive the expression of output voltage. (1 + 4 = 5)
- (c) Explain the following terms of an op-amp : (2 + 2 = 4)
- (i) CMRR
- (ii) Input offset voltage
5. (a) Subtract 14 from 45 using 8 bit 2's complement arithmetic. (4)
- (b) Convert the following : (4 × 1 = 4)
- (i) $(52)_{10}$ to binary
- (ii) $(11011)_2$ to decimal
- (iii) $(110101)_2$ to octal
- (iv) $(1011011011)_2$ to hexadecimal
- (c) Convert the expression $f(A, B, C) = A + ABC$ in standard sop form. Reduce the expression $\sum m(0, 2, 3, 4, 5, 6)$ using K map and implement it using AOI logic. (2 + 5 = 7)
6. (a) Draw a full adder circuit and explain its operation. (7)
- (b) Design a 4:16 decoder from two 3:8 decoder. (3)
- (c) Design a 2bit asynchronous up counter using JR flipflop. (5)
7. (a) What is sensor? List the four factors the need to be considered in selecting a sensor. (5)
- (b) Explain the working principle of techogenerator. (5)
- (c) Illustrate with figures, the three common robotic configurations. (5)

BINA CHOWDHURY CENTRAL LIBRARY
 (BINT & GITS)
 Azara, Haldia, West Bengal,
 G. No. 1077