

Total No. of printed pages = 4

3/1/19

EE 131302

Roll No. of candidate

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BINA CHOWDHURY CENTRAL LIBRARY

(GIMT & GIPS)

Azara, Hatkhawapara,

Guwahati -781017

2019

B.Tech. (EE) 3rd Semester End-Term Examination

CIRCUIT ANALYSIS

(New Regulation)

(w.e.f. 2017-2018)

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer Q.No. 1 and any *four* from the rest.

1. Answer all the questions : (10 × 1 = 10)
 - (i) The no of links of a graph having 8 branches and 6 nodes is _____.
 - (ii) Determinant of the incidence matrix of a closed loop is always _____.
 - (iii) Condition for Reciprocity in Y parameter is _____.
 - (iv) The maximum power that a 10V dc source with an internal resistance of 5 ohm can supply to a resistive load is _____.
 - (v) The time constant of a series RC circuit having dc excitation is given by _____.

[Turn over

(vi) A series R-L circuit has $R = 20 \text{ ohm}$ and $L = 5 \text{ H}$. If a dc voltage of 100 V applied at $t = 0$, the time constant is _____.

(vii) A two port network is defined by the relations

$$V_1 = 5I_1 + 3I_2$$

$$V_2 = 2I_1 - 7I_2$$

The value of Z_{22} will be _____.


(viii) The polynomial $P(s) = 3S^4 + 5S^3 - S^2 + S + 6$ is a hurwitz polynomial. [True/False]

(ix) The branches that are removed from a tree are termed as _____.

(x) A series R-L circuit having $R = 50 \text{ ohm}$ and $L = 10 \text{ H}$ are connected across 200V at $t = 0$. The equation of charging current is _____.


2. (a) Define reduced incidence matrix. What are the properties of incidence matrix? (5)

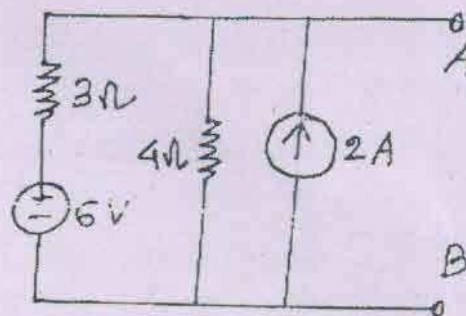(b) Find Millmans equivalent for the left of the terminals A-B. (6)




(c) Write short notes on energy stored in an inductor. (4)

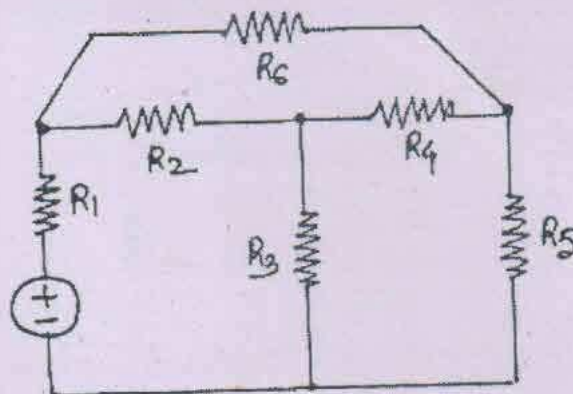
3. (a) Find the fundamental Cut-set matrix for the following network. (8)



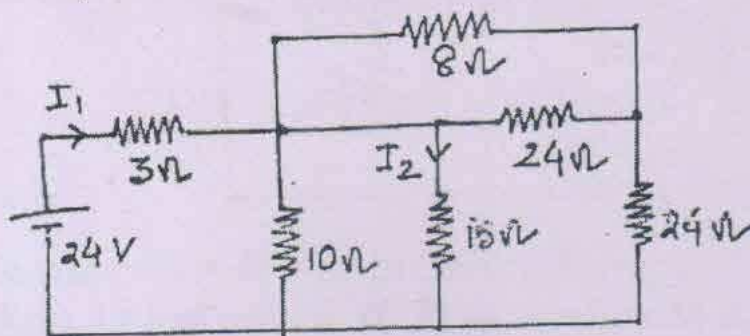- (b) Find I_1 and I_2 of the network using Nodal analysis. (7)




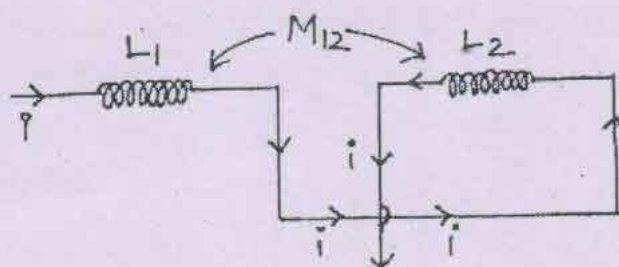4. (a) State and explain Reciprocity theorem. (5)
 (b) Find equivalent inductance for the following circuit. (5)




- (c) The number of turns in two coupled coils are 500 and 1500 respectively. When a current of 5A flows in coil 1, the total flux in the coil is 0.6 mWb and the flux linking the 2nd coil is 0.3 mWb? Find L_1, L_2, M and K . (5)

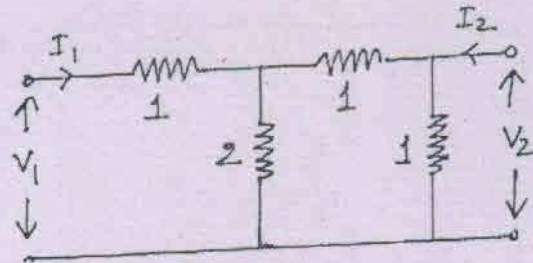5. (a) Find the equivalent Y parameters if 2 two-port networks are connected in parallel. (8)
- (b) Obtain transmission parameters of the network shown in the figure. (7)



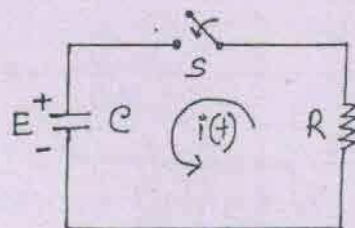6. (a) For the given circuit, find the expression of current $i(t)$. (7)



- (b) A series R-L circuit has $R = 25 \text{ ohm}$ and $L = 5 \text{ H}$. A dc voltage of 100 V is applied at $t = 0$. Find
- the equation of charging current ($4 \times 2 = 8$)
 - voltage across R and L
 - the current in the circuit 0.5 Sec later.
 - the time at which the drop across R and L are same.

7. (a) A reduced incidence matrix is given by

$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

Obtain the number of possible trees. (5)

- (b) Find the 1st and 2nd Foster form of the driving point impedance function. (5 + 5 = 10)

$$z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$