

Enrolment Number										
------------------	--	--	--	--	--	--	--	--	--	--

Total No. of printed pages = 03

Monsoon, 2023
B.C.A Semester Examinations
DIGITAL LOGIC
Course Code: BCA23102T

Full Marks – 60

Time – 2 ½ hours

The figure in the margin indicates full marks for the questions.

Part A

Answer ALL questions

Multiple Choice(10 x 1mark = 10marks)

1. a) Largest Unsigned Binary number can be stored in a 8 bit register is
 - (i) 127
 - (ii) 128
 - (iii) 255
 - (iv) 256
- b) In Boolean algebra if $A+1=1$ then the value of A is
 - (i) 1
 - (ii) 0
 - (iii) 1 or 0
 - (iv) None of the these
- c) The even parity bit for 1011 1011 is
 - (i) 1
 - (ii) 0
 - (iii) 1 or 0
 - (iv) None of the these
- d) The gray code for 1101
 - (i) 1011
 - (ii) 1010
 - (iii) 0010
 - (iv) None of these
- e) if $F1(ABC)=\sum (0,1,2,3)$ and $F2(ABC)=\sum (4,5,6,7)$ then
 - (i) $F1(ABC)=F2(ABC)$
 - (ii) $F1(ABC)+F2(ABC)=1$
 - (iii) $\{F1(ABC)\} \neq \{F2(ABC)\}$
 - (iv) None of the these
- f) Which is not an Universal gate
 - (i) NOR gate
 - (ii) NAND gate
 - (iii) EXOR gate

- (iv) All of these
- g) Which is a register
 - (i) MAR
 - (ii) Program Counter
 - (iii) Accumulator
 - (iv) All of these
- h) To address 1000 locations we need an address size of
 - (i) 8 bits
 - (ii) 9 bits
 - (iii) 10 bits
 - (iv) 11 bits
- i) Random Access Memory is a
 - (i) Volatile memory
 - (ii) Semiconductor memory
 - (iii) Main memory
 - (iv) All of these
- j) The number -7 in -8421 code is
 - (i) 1001
 - (ii) 1100
 - (iii) 1010
 - (iv) 1011

Part B

Answer ANY FOUR questions
(4x 5 mark = 20 marks)

2. Convert

- (i) Decimal number -128.50 into binary
- (ii) Hexadecimal number 1A1B in to Octal

3. Add

- (i) Binary numbers 1011, 1001, 1111, 1100
- (ii) BCD the numbers 0111 and 0101

4. Simplify using 2's complement

- (i) $-12 + 13$
- (ii) $-12 - 13$

5. Draw the NOR-NOR Circuit for the following:

$$F(ABC) = AB + BC + CA$$

6. Represent the following functions using a Decoder and OR gates

$$F1(xyz) = xyz'$$

$$F2(xyz) = \sum(5,6,7)$$

7. What is the problem of SR flip – flop ? How it is solved using D Flip flop? Explain with diagrams.

Part C

Answer ANY TWO questions
(2 x10 mark = 20 marks)

8. a) Reduce the Given Boolean function using k-map
 $F(WXYZ) = F(0,1, 2,4,6,8,9,10,12,14)$
b) Design a counter for the following outputs using T flip flop
1,3,4,5,7 and repeat
9. a) Draw a 8X1 multiplexer and explain its working principle.
b) Draw the excitation table for SR flip flop and explain.
- 10 a) What is Master Slave flip flop. Draw the diagram for JK master slave flip flop and explain it.
b) Represent -135 in IEEE 32 bit floating point representation.

Part D

Short Notes
(2 x5 mark = 10marks)

11. Write any two :
- a) Full Adder and its working principle
 - b) Binary Cell and its working principle
 - c) Postulates of Boolean algebra
 - d) Designing a 4X4 ROM
